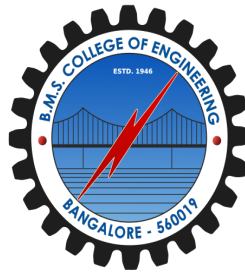


**AIC SELF STUDY [15ES4GCAIC]**  
*in*  
**ELECTRONICS AND COMMUNICATION ENGINEERING**

*by*  
**A. Vipula                      Akshit Bhalla                      Amrutha M.**  
*[1BM16EC007]                      [1BM16EC015]                      [1BM16EC018]*

*Under the supervision of*  
**Dr. D. Seshachalam**



**Department of Electronics and Communication Engineering**  
**B.M.S COLLEGE OF ENGINEERING, Basavanagudi**  
**Bangalore-560019, India**

## Question 1

Plot the frequency response curve for any practical circuit using 741 op-amp and verify the following equation:

$$(Bandwidth * Gain)_{openloop} = (Bandwidth * Gain)_{closedloop}$$

### Solution

We solve each solution algebraically to determine a possible constant  $c$ .

#### Part One

$$\begin{aligned} n^2 + n + 1 &= \\ &\leq n^2 + n^2 + n^2 \\ &= 3n^2 \\ &\leq c \cdot 2n^3 \end{aligned}$$

Thus a valid  $c$  could be when  $c = 2$ .

#### Part Two

$$\begin{aligned} n^2 + n\sqrt{n} &= \\ &= n^2 + n^{3/2} \\ &\leq n^2 + n^{4/2} \\ &= n^2 + n^2 \\ &= 2n^2 \\ &\leq c \cdot n^2 \end{aligned}$$

Thus a valid  $c$  is  $c = 2$ .

#### Part Three

$$\begin{aligned} n^2 - n + 1 &= \\ &\leq n^2 \\ &\leq c \cdot n^2/2 \end{aligned}$$

Thus a valid  $c$  is  $c = 2$ .

**Question 2**

Calculate various DC and AC electrical parameters for a given OPAMP and verify the same with various datasheet.

**Solution**

**Question 3**

Design and simulate working of an Instrumentation amplifier for measuring temp change using wheat-stone bridge and instrumentation amplifier.

**Solution**

## Question 4

Design and Simulate a V to I converter with grounded load for an application. Measure sensitivity of the circuit.

## Solution

## Question 5

Design and Simulate an experiment to Plot transfer characteristics of any practical op-amp.

### Solution

#### Inverting Open Loop Configuration

- The practical Operational Amplifier LM101A was used for this simulation experiment.

The circuit can be constructed as show in Figure 1.

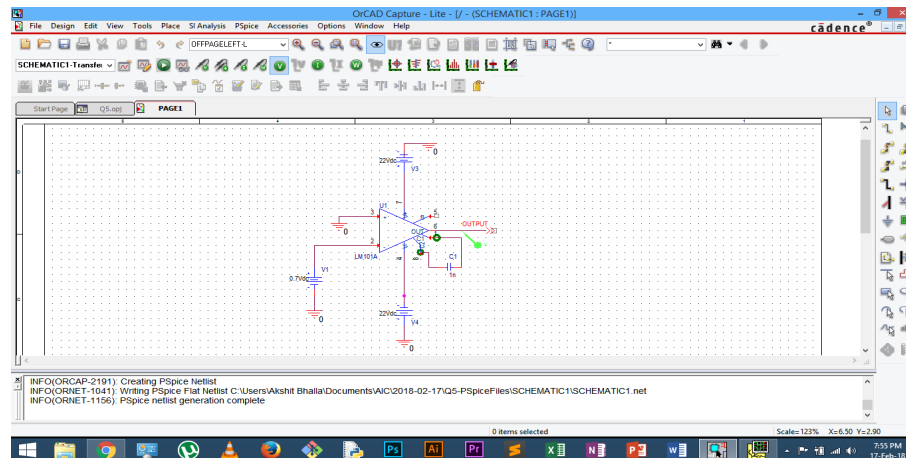


Figure 1: Circuit Diagram

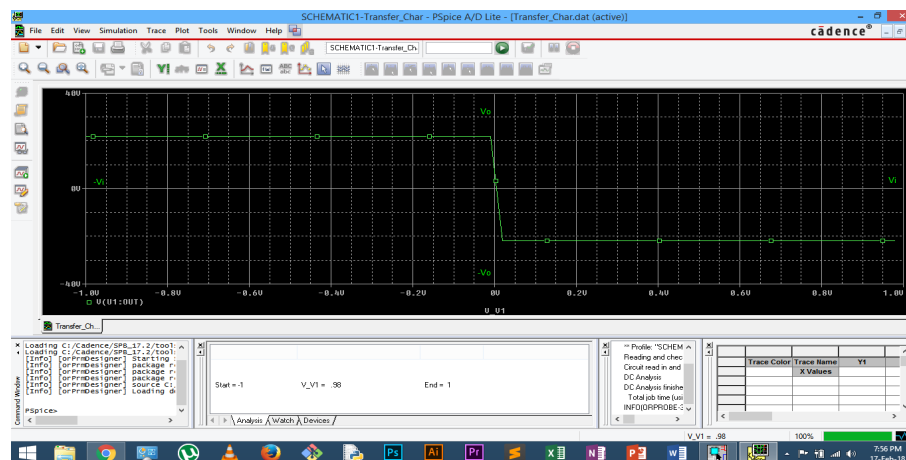


Figure 2: Transfer Characteristics

## Open Loop Configuration with Inverting and Non-Inverting Inputs - 1

The circuit can be constructed as show in Figure 3.

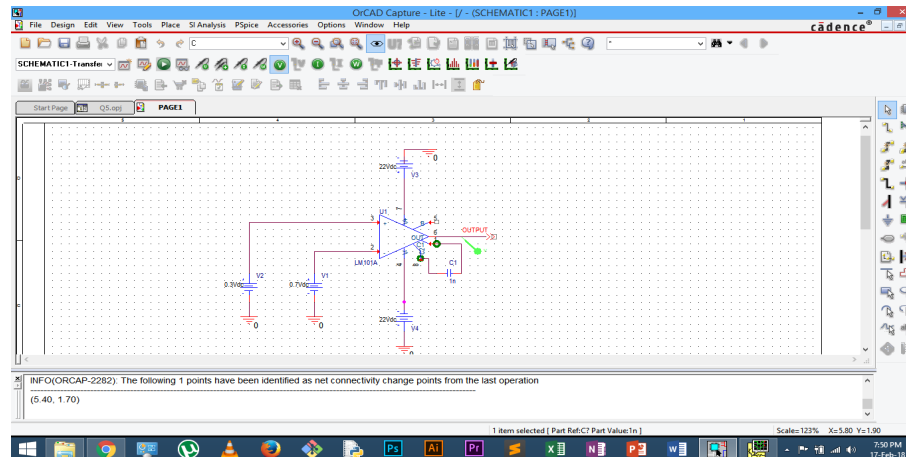


Figure 3: Circuit Diagram

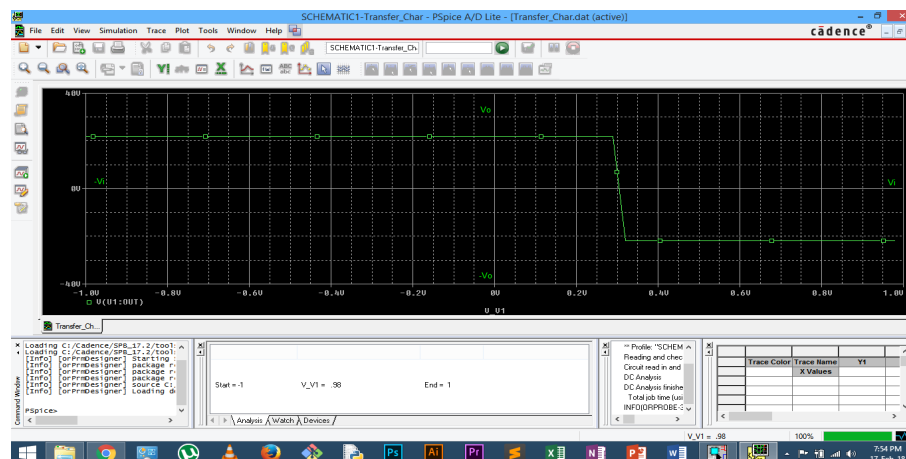


Figure 4: Transfer Characteristics

## Open Loop Configuration with Inverting and Non-Inverting Inputs - 2

The circuit can be constructed as show in Figure 5.

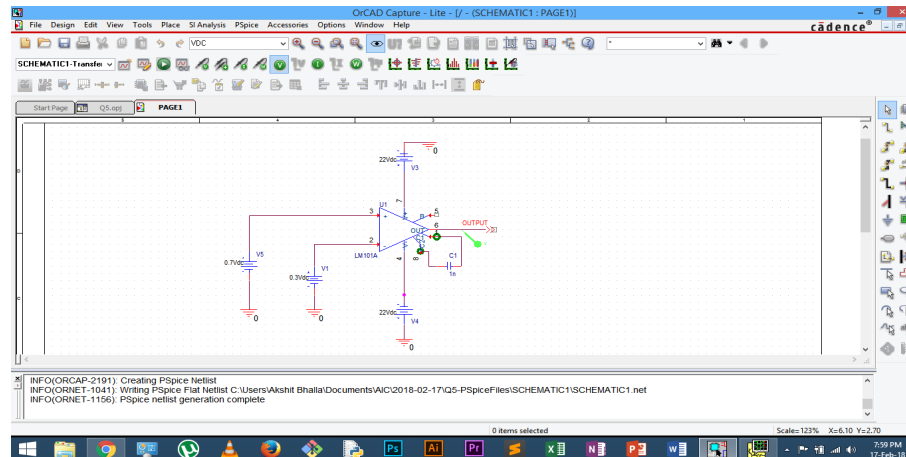


Figure 5: Circuit Diagram

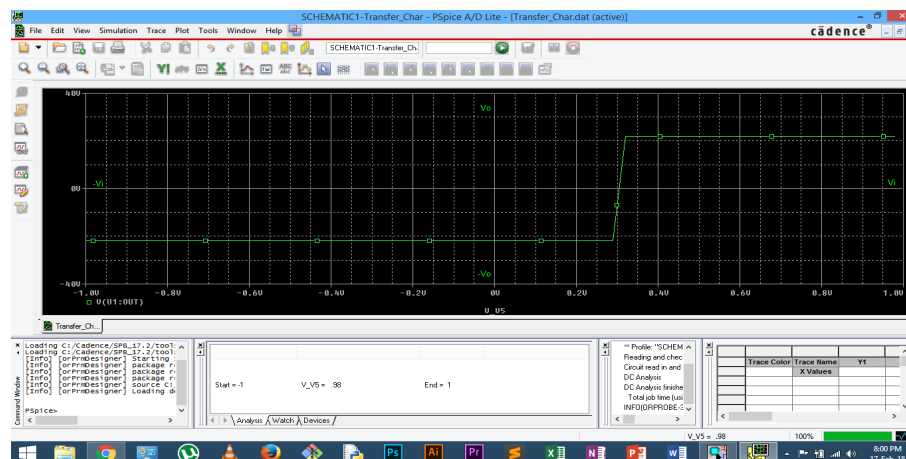


Figure 6: Transfer Characteristics