

ANALOG INTEGRATED CIRCUITS [15ES4GCAIC]
SELF STUDY
in
ELECTRONICS AND COMMUNICATION ENGINEERING
by

A. Vipula

[1BM16EC007]

Akshit Bhalla


[1BM16EC015]

Amrutha M.

[1BM16EC018]

Under the supervision of

Dr. D. Seshachalam

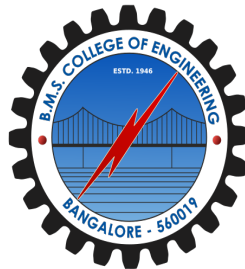

February 28th, 2018

Department of Electronics and Communication Engineering

B.M.S COLLEGE OF ENGINEERING, Basavanagudi

Bangalore-560019, India

Question 1

Plot the frequency response curve for any practical circuit using 741 op-amp and verify the following equation:

$$(Bandwidth * Gain)_{openloop} = (Bandwidth * Gain)_{closedloop}$$

Solution

For Open Loop configuration, the $Bandwidth * Gain = 5 \times 2 \times 10^5 = 1MHz$

Gain is represented in decibels. $Gain_{dB} = 20 \log_{10} Gain$

We have used Bode plot to represent the plot of $|Gain|$ vs. $Frequency$

The circuit shown is an inverting amplifier.

From the graph, in Closed Loop configuration:

- $Bandwidth = 96.619kHz$
- $Gain = 10^{22.973/20} = 14.081$

$$\therefore (Bandwidth * Gain)_{closedloop} = 1.36MHz \approx (Bandwidth * Gain)_{openloop}$$

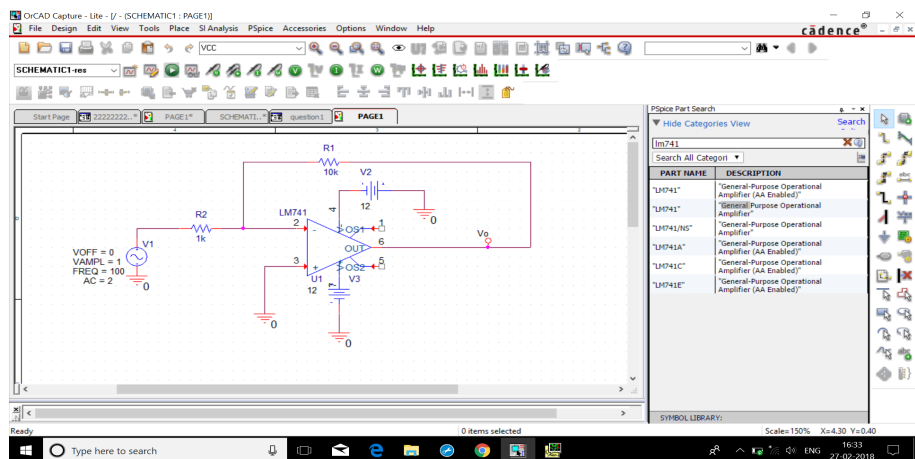


Figure 1: Circuit Diagram

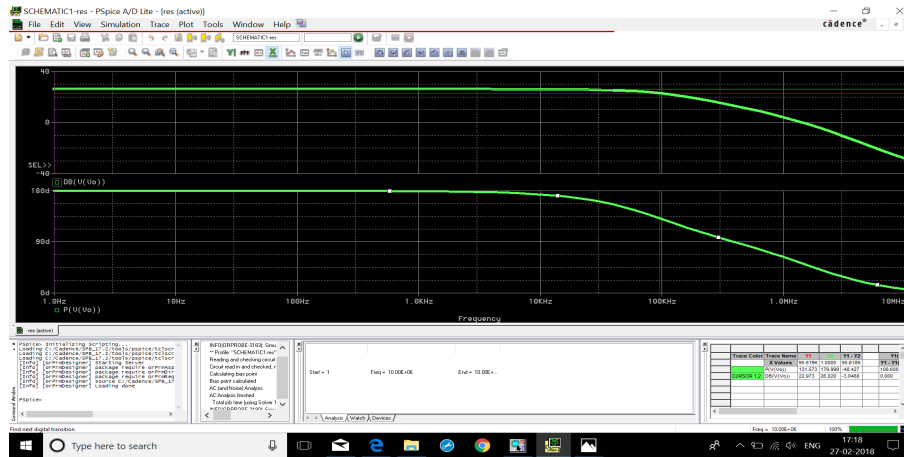


Figure 2: Graph

Question 2

Calculate various DC and AC electrical parameters for a given OPAMP and verify the same with various datasheet.

Solution

The Operational Amplifier used is LM358NS. Bias Point Analysis was performed in order to obtain the DC parameters of the circuit. Current and Voltage readings in every branch have been found.

- Input Bias Current $I_B = \frac{-48.23nA - 41.70nA}{2} = -44.965nA$
- Input Offset Current $I_{OS} = -41.70nA - (-48.23nA) = 6.53nA$
- Input Offset Voltage $V_{OS} = 3mV$, $V_{Output} = 962.2\mu V \approx 0V$

The values obtained are verified as per the datasheet given below.

6.5 Electrical Characteristics for LMx58
at specified free-air temperature, $V_{CC} = 5V$ (unless otherwise noted)

PARAMETER	TEST CONDITIONS ⁽¹⁾	T _A ⁽²⁾	LM358 LM258			LM358			UNIT
			MIN	TYP ⁽³⁾	MAX	MIN	TYP ⁽³⁾	MAX	
V_{IO}	Input offset voltage	$V_{CC} = 5V$ to MAX, $V_{IO} = V_{OS(max)}$, $V_D = 1.4V$		5	5		3	7	mV
μV_{IO}	Average temperature coefficient of input offset voltage	Full range		7	7		7	9	$\mu V/^\circ C$
I_{IO}	Input offset current	$V_D = 1.4V$		2	30		2	50	nA
μI_{IO}	Average temperature coefficient of input offset current	Full range		100			10	150	$\mu A/^\circ C$
I_B	Input bias current	$V_D = 1.4V$							nA
		Full range			-20		-20	-250	
					-300			-500	
V_{CM}	Common-mode input voltage range	$V_{CC} = 5V$ to MAX							V
		Full range							
V_{OH}	High-level output voltage	$R_L \geq 2k\Omega$ $V_{CC} = MAX$							V
		Full range							
V_{OL}	Low-level output voltage	$R_L \leq 10k\Omega$ $V_{CC} = MAX$							mV
A_{VOL}	Large-signal differential voltage amplification	$V_{CC} = 5V$ to MAX, $V_D = 1V$ to $11V$, $R_L \geq 2k\Omega$							V/mV
		Full range							
CMRR	Common-mode rejection ratio	$V_{CC} = 5V$ to MAX, $V_D = V_{OS(max)}$							dB
k_{PSRR}	Supply-voltage rejection ratio ($\Delta V_{IN}/\Delta V_{CC}$)	$V_{CC} = 5V$ to MAX							dB
V_{out}/V_{in}	Crosstalk attenuation	$f = 1kHz$ to $20kHz$							dB
I_O	Output current	$V_{CC} = 15V$, $V_D = 1V$, $V_{IO} = 0V$							mA
		Source							
		Sink							
I_{SC}	Short-circuit output current	$V_{CC} = 5V$, GND at $-5V$, $V_D = 0V$							mA

Figure 3: Datasheet of LM358 Operational Amplifier

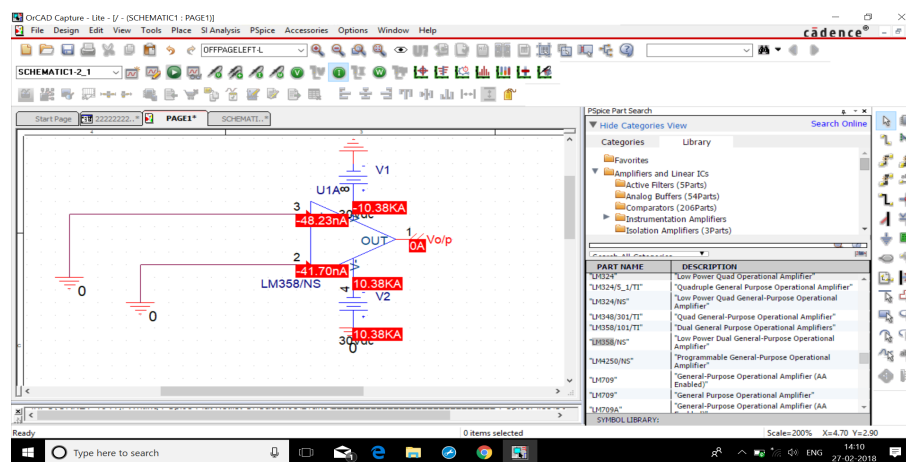


Figure 4: Circuit Diagram with Current Markers

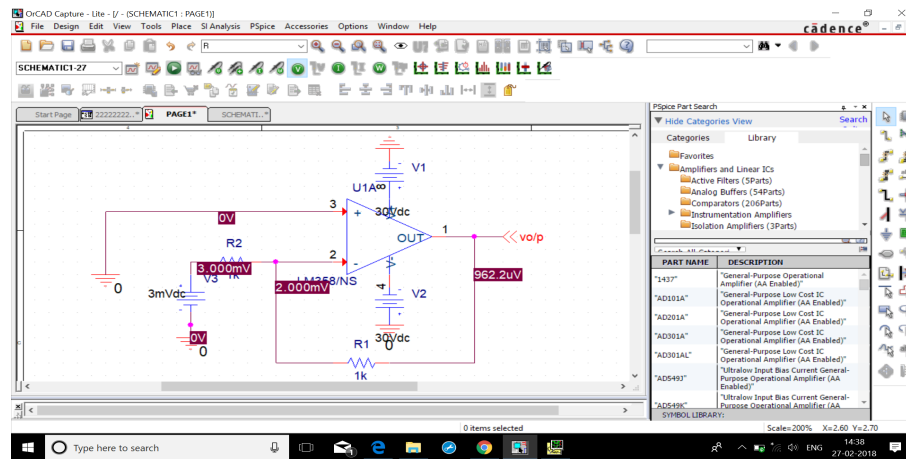


Figure 5: Circuit Diagram with Voltage Markers

Question 3

Design and simulate working of an Instrumentation amplifier for measuring temp change using wheat-stone bridge and instrumentation amplifier.

Solution

- R_4 is the Resistor which is the parameter under consideration.
- The resistance parameter is varied by graphical conditions. The resistor is analogue to the temperature.
- Assume, $R_1, R_2, R_3 = 100\Omega$ Initially $R_4 = 50\Omega$
Assume $Gain(G) = 10 \therefore R_G = 49.4k/(G - 1) = 5.488k\Omega$
- Due to supply voltage limiting factor the output of instrumentation saturates for $R_4 < 72\Omega$

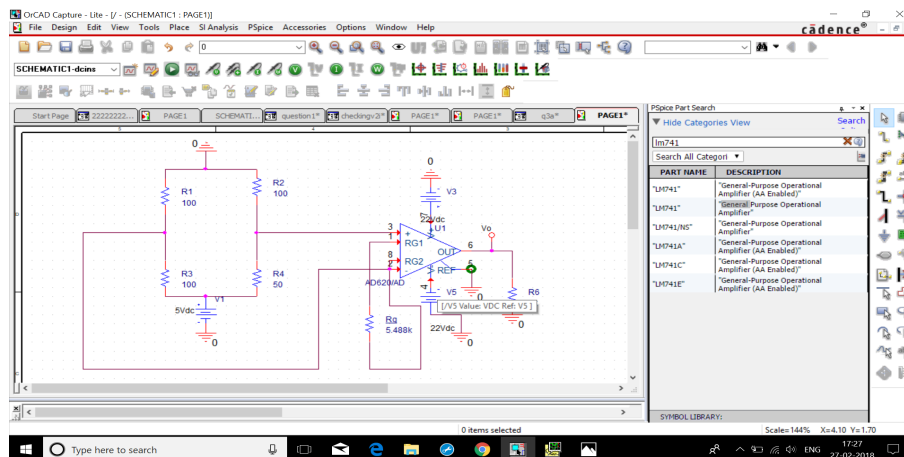


Figure 6: Circuit Diagram

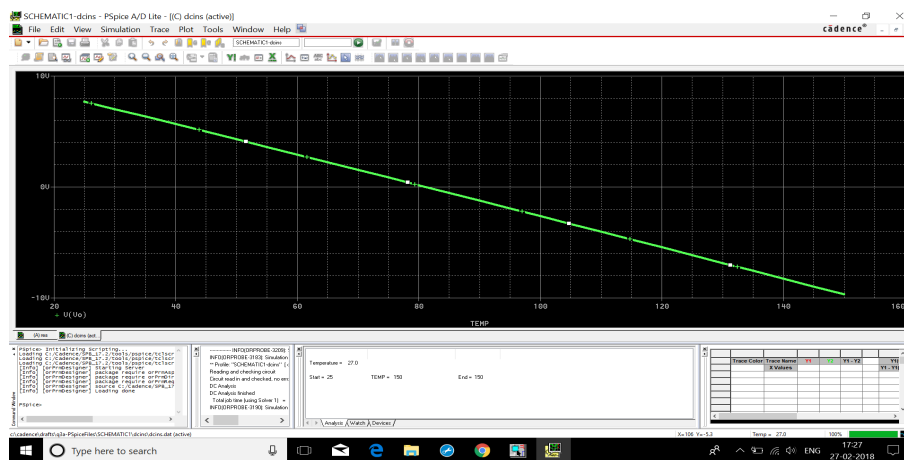


Figure 7: Graph

Question 4

Design and Simulate a V to I converter with grounded load for an application. Measure sensitivity of the circuit.

Solution

- The Operational Amplifier used is LM741 and the application specified in this circuit is an LED Tester.
- The LED and the Load Resistance are connected in parallel to each other.
- The Op-Amp is sensing the input voltage thereby producing the output voltage which in turn produces a current flowing through the load.
where, $I_L = V_i/R_f$
- The LED glows when required amount of current flows through it. The current flowing through the LED is 0.849 mA .

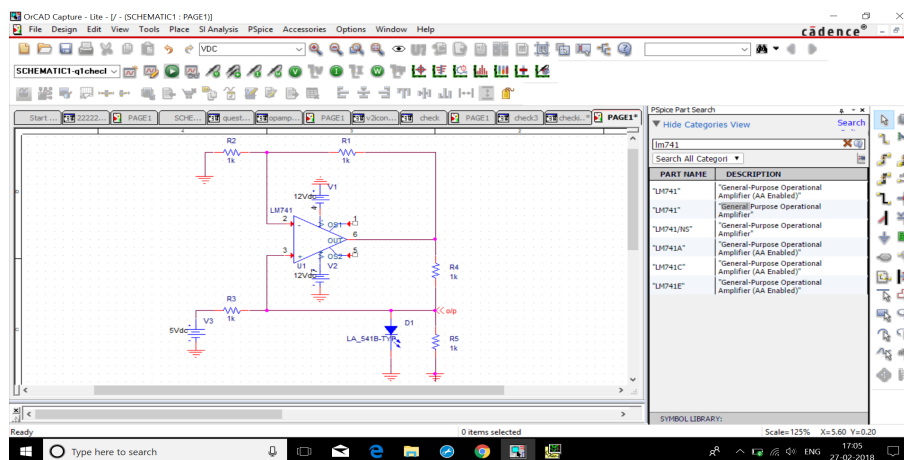


Figure 8: Circuit Diagram

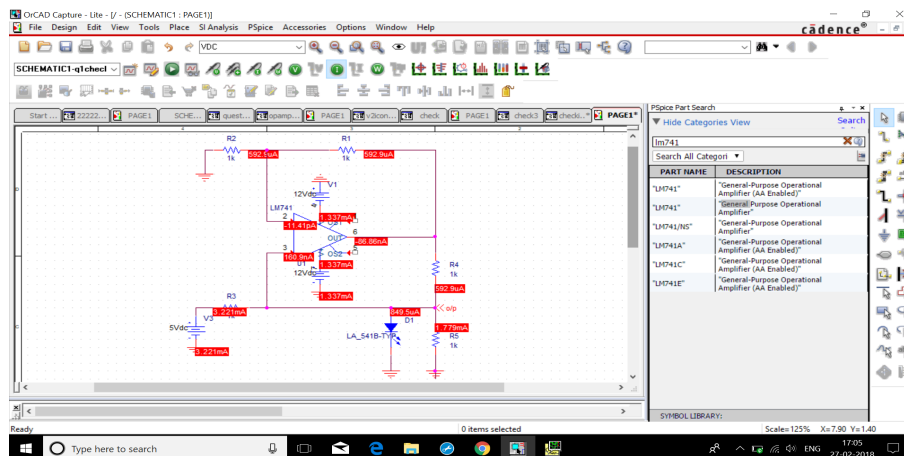


Figure 9: Circuit Diagram with Current Markers

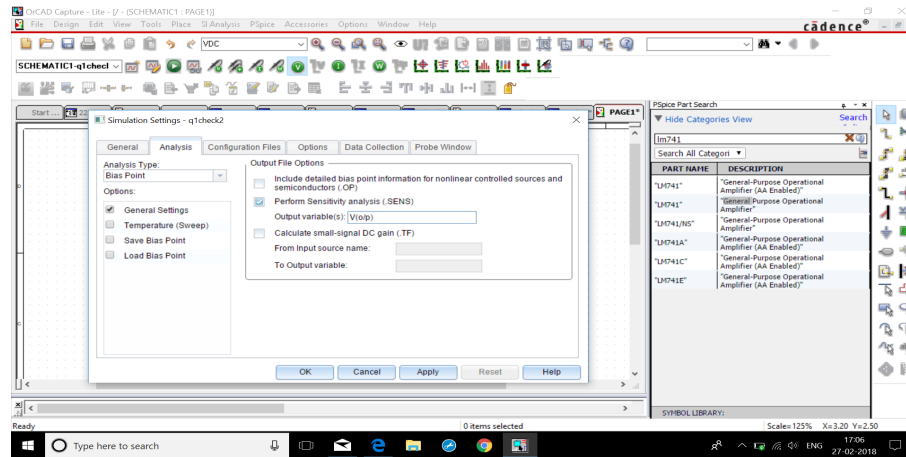


Figure 10: Simulation Settings

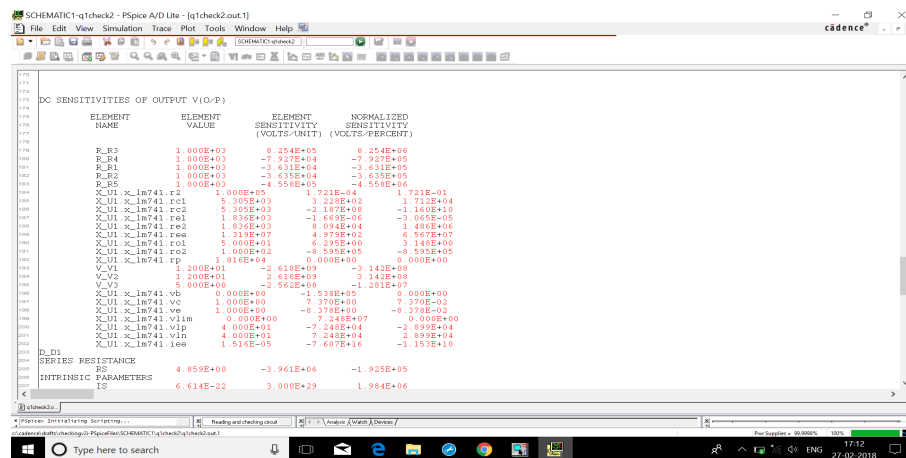


Figure 11: Output File

Question 5

Design and Simulate an experiment to Plot transfer characteristics of any practical amp.

Solution

Inverting Open Loop Configuration

- The practical Operational Amplifier LM101A was used for this simulation experiment
- An input voltage of 0.7 V is provided to the inverting terminal. The non-inverting terminal is grounded.
- The circuit was constructed as show in Figure 12.

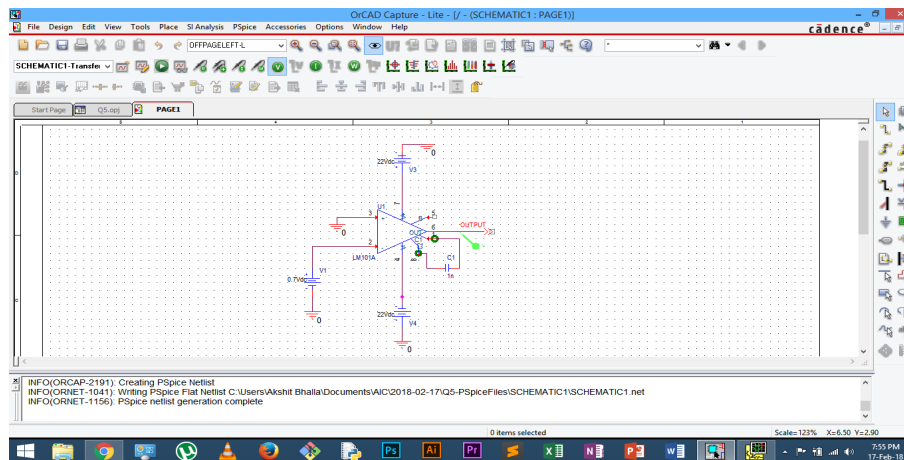


Figure 12: Circuit Diagram

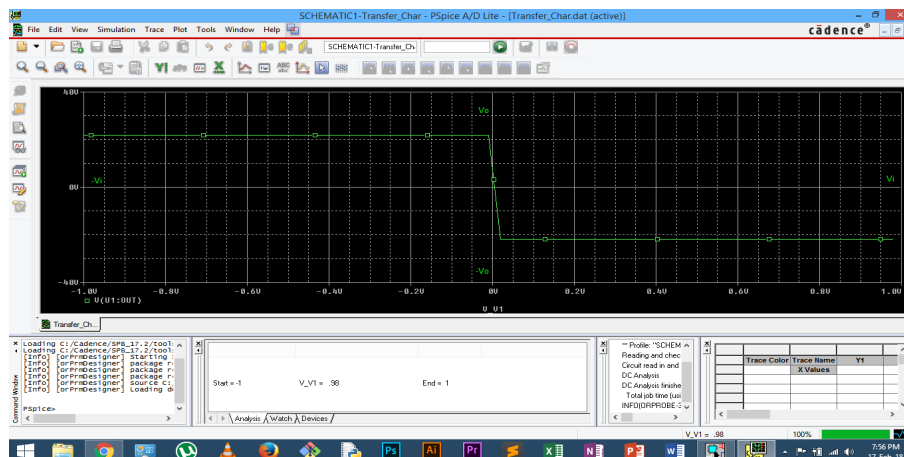


Figure 13: Transfer Characteristics

Open Loop Configuration with Inverting and Non-Inverting Inputs - 1

- The practical Operational Amplifier LM101A was used for this simulation experiment
- An input voltage of 0.7 V is provided to the inverting terminal and 0.3 V to the non-inverting terminal.
 $V_{inv} > V_{non-inv}$
- The circuit was constructed as show in Figure 14.

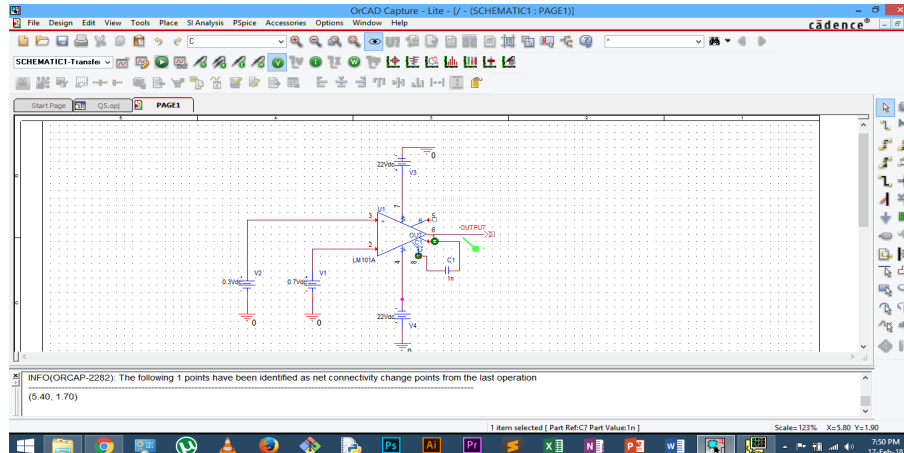


Figure 14: Circuit Diagram

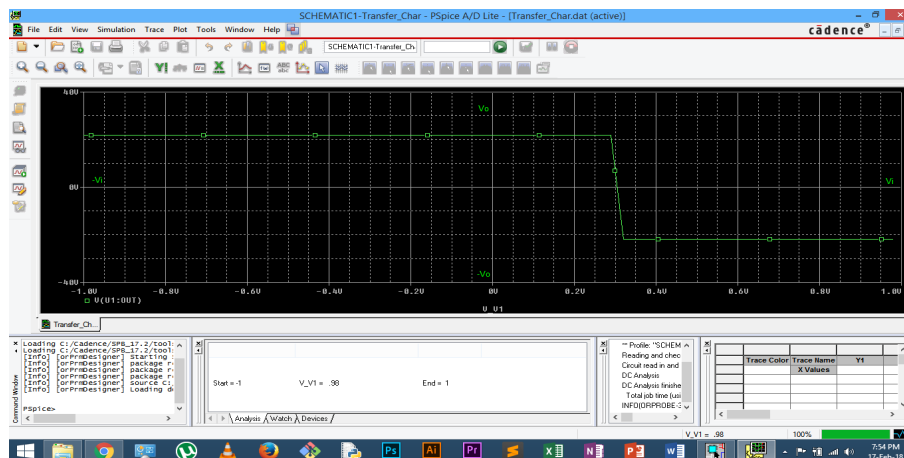


Figure 15: Transfer Characteristics

Open Loop Configuration with Inverting and Non-Inverting Inputs - 2

- The practical Operational Amplifier LM101A was used for this simulation experiment
- An input voltage of 0.3 V is provided to the inverting terminal and 0.7 V to the non-inverting terminal.
 $V_{inv} < V_{non-inv}$
- The circuit was constructed as show in Figure 16.

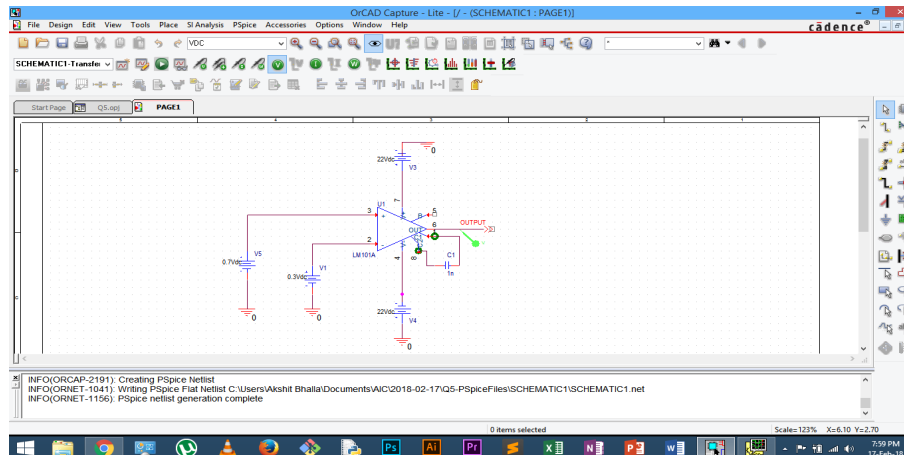


Figure 16: Circuit Diagram

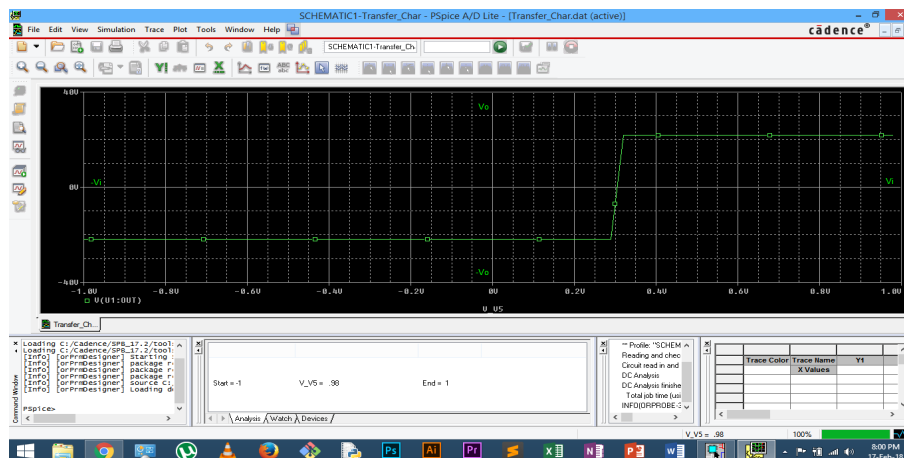


Figure 17: Transfer Characteristics

Conclusion

- Graphs for open loop gain and closed loop gain could not be merged together on the same graph.
- The Op-Amp could not be modeled internally to change the pre-defined parameters.
- The 3 Op-Amp instrumentation amplifier could not be simulated since the maximum number of nodes in the circuit should be ≈ 75 . Instead a built-in instrumentation amplifier was used.